

Full Subtractor :

- Full subtractor performs subtraction of three binary bits
1. minuend bit A
 2. Subtrahend bit B
 3. borrow-in bit B_{in}
- It produces two outputs, the difference bit D
1. borrow-out bit B_{out}
- minuend - the bit to be subtracted from
- Subtrahend - the bit to subtract
- B_{in} - Borrow from the previous lower significant bit.

Truth Table

| | B | B _{in} | D | B _{out} |
|---|---|-----------------|---|------------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Boolean Expression

$$D = A \oplus B \oplus B_{in}$$

$$B_{out} = \bar{A}(B \oplus B_{in}) + B \cdot B_{in}$$

Gate level

